

## Lab 7 – Improved Barrel Counter

Group G

Chang, Philbert (013179257)

Hua, Russell (013184015)

Thai, Paul (014760252)

Professor Aly

ECE 3300L.01

August 09, 2021

## Problem

For this lab, the task is to create a modified and improved up down counter that could take in a load from four switches and display it onto the seven-segment display according to the selects. The way the FPGA is mapped out, there is a switch for the counter to go up or down. There is a switch that would enable to be the count to start and stop. There are three switches for the select, four for the input that is being loaded in, and then five that control the speed of the counter.

## Code Detail

The code uses a lot of modules to achieve this task. There is the top module that brings everything in together. The SSD module is meant for displaying the values of the counter on the seven-segment display. The clk\_divider module is used to change the speed of the clock. Inside of the BCD\_32\_bit module there are sub modules that controls the count, the selects, and the input that would allow us to complete this lab in the manner that the professor explained in his video.

```
--
23 module top(
24     input clk,
25     input reset,
26     input [4:0] SW,
27     input enable,
28     input up_down,
29     input load,
30     input [3:0] in,
31     input [2:0] select,
32     output wire [6:0] a_to_g,
33     output wire [7:0] an,
34     output wire dp
35 );
36
37 wire temp1;
38 clk_divider GEN(
39     .clk(clk),
40     .reset(reset),
41     .SW(SW),
42     .clk_div(temp1)
43 );
44
45 wire [31:0] temp2;
46
47 BCD_32_bit BCD(
48     .clk(temp1),
49     .reset(reset),
50     .en(enable),
51     .up_down(up_down),
52     .load(load),
53     .in(in),
54     .select(select),
55     .set(temp2)
56 );
57
58 ssd display(
59     .SW(temp2),
60     .clk(clk),
61     .reset(reset),
62     .a_to_g(a_to_g),
63     .an(an),
64     .dp(dp)
```

```

58     ssd display(
59         .SW(temp2),
60         .clk(clk),
61         .reset(reset),
62         .a_to_g(a_to_g),
63         .an(an),
64         .dp(dp)
65     );
66
67 endmodule

```

*Figures 1: Verilog code - top*

```

21 `define dp_off 1'b1
22 `define initial_digit 8'b11111111
23
24 module ssd(
25     input [31:0] SW,
26     input clk,
27     input reset,
28     output reg [6:0] a_to_g,
29     output reg [7:0] an,
30     output wire dp
31 );
32
33 assign dp = `dp_off;
34
35 wire [2:0] s;
36 wire [7:0] aen;
37 reg [19:0] clkdiv;
38 reg [3:0] digit;
39 assign s = clkdiv[19:17];
40 assign aen = `initial_digit;
41
42
43
44 // clock divider
45 always@(posedge clk or posedge reset)
46 begin
47     if (reset)
48         clkdiv <= 0;
49     else
50         clkdiv <= clkdiv+1;
51     end
52
53 // digit select :ancode
54 always@(aen, s)
55 begin
56     an = 8'b11111111;
57     if(aen[s] == 1)
58         an[s] = 0;
59     end
60
61 // 4-to-1 Mux: mux4x1
62 always@(s, SW)

```

```

60 :
61 : // 4-to-1 Mux: mux4x1
62 : always@(s, SW)
63 : begin
64 :     case(s)
65 :         0: digit = SW[3 : 0];
66 :         1: digit = SW[7 : 4];
67 :         2: digit = SW[11: 8];
68 :         3: digit = SW[15:12];
69 :         4: digit = SW[19:16];
70 :         5: digit = SW[23:20];
71 :         6: digit = SW[27:24];
72 :         7: digit = SW[31:28];
73 :         default: digit = 4'bZZZ;
74 :     endcase
75 : end
76 :
77 : // 7-segment decoder : hex7seg
78 :
79 : always@(digit)
80 : begin
81 :     case(digit)
82 :         0: a_to_g = 7'b0000001;
83 :         1: a_to_g = 7'b1001111;
84 :         2: a_to_g = 7'b0010010;
85 :         3: a_to_g = 7'b0000110;
86 :         4: a_to_g = 7'b1001100;
87 :         5: a_to_g = 7'b0100100;
88 :         6: a_to_g = 7'b0100000;
89 :         7: a_to_g = 7'b0001111;
90 :         8: a_to_g = 7'b0000000;
91 :         9: a_to_g = 7'b0000100;
92 :
93 :         default: a_to_g = 7'b0000100;
94 :     endcase
95 : end
96 :
97 :
98 : endmodule

```

*Figures 2: Seven segment display*

```

22 module clk_divider(
23     input clk,
24     input reset,
25     input [4:0] SW,
26     output reg clk_div
27 );
28
29     reg [31:0] count;
30
31 always@(posedge clk or posedge reset)
32 begin
33     if (reset)
34         count <= 0;
35     else
36         count <= count + 1;
37 end
38
39     integer i;
40 always@(posedge clk or posedge reset)
41 begin
42     if (reset)
43         clk_div <= 1'b0;
44     else
45     begin
46         for (i = 0; i < 32; i = i + 1)
47             if (SW == i)
48                 clk_div <= count[i];
49     end
50 end
51
52 endmodule

```

*Figure 3: Clock divider*

```

23 module BCD_32_bit(
24     input clk,
25     input reset,
26     input en,
27     input up_down,
28     input load,
29     input [3:0] in,
30     input [2:0] select,
31     output wire [31:0] set
32 );
33
34 wire [7:0] temp;
35 wire [31:0] temp_select;
36
37 assign temp[0] = en;
38
39 genvar i;
40
41 demux_DB data (
42     .in(in),
43     .select(select),
44     .out(temp_select)
45 );
46
47 generate
48 for (i = 0; i<8 ; i = i+1)
49 begin
50     counter count(
51         .clk(clk),
52         .reset(reset),
53         .enable_in(temp[i]),
54         .up_down(up_down),
55         .load(load),
56         .in0(temp_select[i]),
57         .in1(temp_select[i + 8]),
58         .in2(temp_select[i + 16]),
59         .in3(temp_select[i + 24]),
60         .set(set [4*(i+1)-1 : 4*i]),
61         .enable_out(temp[i+1])
62     );
63 end
64 endgenerate
65
66 endmodule

```

*Figure 4: BCD 32 bit*

```

23 module counter(
24     input clk,
25     input reset,
26     input enable_in,
27     input up_down,
28     input load,
29     input in0,
30     input in1,
31     input in2,
32     input in3,
33     output reg [3:0] set,
34     output wire enable_out
35 );
36
37 wire [3:0] in;
38 assign in[0] = in0;
39 assign in[1] = in1;
40 assign in[2] = in2;
41 assign in[3] = in3;
42
43 always@(posedge clk or posedge reset or posedge load)begin
44     if (reset)begin
45         if (up_down)
46             set <= 4'd9;
47         else
48             set <= 4'd0;
49     end
50     else if (load)
51         set <= in;
52     else begin
53         if (enable_in)begin
54             if (up_down== 1'b1)begin
55                 if (set > 0)
56                     set <= set - 1;
57             else
58                 set <= 4'd9;
59             end
60         else begin
61             if(set <9)
62                 set <= set+ 1;
63             else
64
65         else begin
66             if(set <9)
67                 set <= set+ 1;
68             else
69                 set <= 4'd0;
70         end
71     end
72 end
73
74 // checks if the current counter value will result in carry to the next counter
75 assign enable_out = ((set[3] & set[0] & (~set[2]) & (~set[1]) & (~up_down)) | ( (~set[3]) & (~set[0]) & (~set[2]) & (~set[1]) & (up_down))) & enable_in ;
76 endmodule

```

*Figures 5: Counter (1 BCD)*

```

22 //databus for the multiplexer
23 module demux_DB(
24     input [3:0] in,
25     input [2:0] select,
26     output wire [31:0] out
27 );
28
29 generate
30 for (genvar i = 0; i < 4; i = i + 1)
31     begin: DEMUXS
32         demux_3_to_8 setter(
33             .in(in[i]),
34             .select(select),
35             .out(out[8*i + 7 : 8 * i])
36         );
37     end
38 endgenerate
39
40 endmodule

```

Figure 6: Demux\_DB

```

23 module demux_3_to_8(
24     input in,
25     input [2:0] select,
26     output wire [7:0] out
27 );
28 assign out[0] = in & ~select[0] & ~select[1] & ~select[2];
29 assign out[1] = in & select[0] & ~select[1] & ~select[2];
30 assign out[2] = in & ~select[0] & select[1] & ~select[2];
31 assign out[3] = in & select[0] & select[1] & ~select[2];
32 assign out[4] = in & ~select[0] & ~select[1] & select[2];
33 assign out[5] = in & select[0] & ~select[1] & select[2];
34 assign out[6] = in & ~select[0] & select[1] & select[2];
35 assign out[7] = in & select[0] & select[1] & select[2];
36
37 endmodule

```

Figure 7: Demux 3x8



```

23 module top_tb(
24
25 );
26     reg clk_tb;
27     reg reset_tb;
28     reg [4:0] SW_tb;
29     reg enable_tb;
30     reg up_down_tb;
31     reg load_tb;
32     reg [3:0] in_tb;
33     reg [2:0] select_tb;
34     wire [6:0] a_to_g_tb;
35     wire [7:0] an_tb;
36     wire dp_tb;
37     integer i;
38     top test_top(
39         .clk      (clk_tb      ),
40         .reset    (reset_tb    ),
41         .SW       (SW_tb       ),
42         .enable   (enable_tb   ),
43         .up_down  (up_down_tb  ),
44         .load     (load_tb     ),
45         .in       (in_tb       ),
46         .select   (select_tb   ),
47         .a_to_g   (a_to_g_tb   ),
48         .an       (an_tb       ),
49         .dp       (dp_tb       )
50     );
51
52 initial begin
53     clk_tb = 0;
54     reset_tb = 1;
55     enable_tb = 0;
56     up_down_tb = 0;

```

```

52 ○ initial begin
53 ○     clk_tb = 0;
54 ○     reset_tb = 1;
55 ○     enable_tb = 0;
56 ○     up_down_tb = 0;
57 ○     load_tb = 0;
58 ○     SW_tb = 0;
59 ○     in_tb = 0;
60 ○     select_tb = 0;
61 ○ end
62 ○ initial begin
63 ○     forever begin
64 ○         #10 clk_tb = ~clk_tb;
65 ○     end
66 ○ end
67 ○ initial begin
68 ○     #10 reset_tb = 0;
69 ○     for (i = 0; i < 32768; i = i + 1) begin
70 ○         #10 SW_tb = i[4:0];
71 ○         enable_tb = i[5];
72 ○         up_down_tb = i[6];
73 ○         load_tb = i[7];
74 ○         in_tb = i[11:8];
75 ○         select_tb = i[14:12];
76 ○     end
77 ○     #100 $finish;
78 ○ end
79 ○ endmodule

```

Figures 8: Testbench

## Flowchart

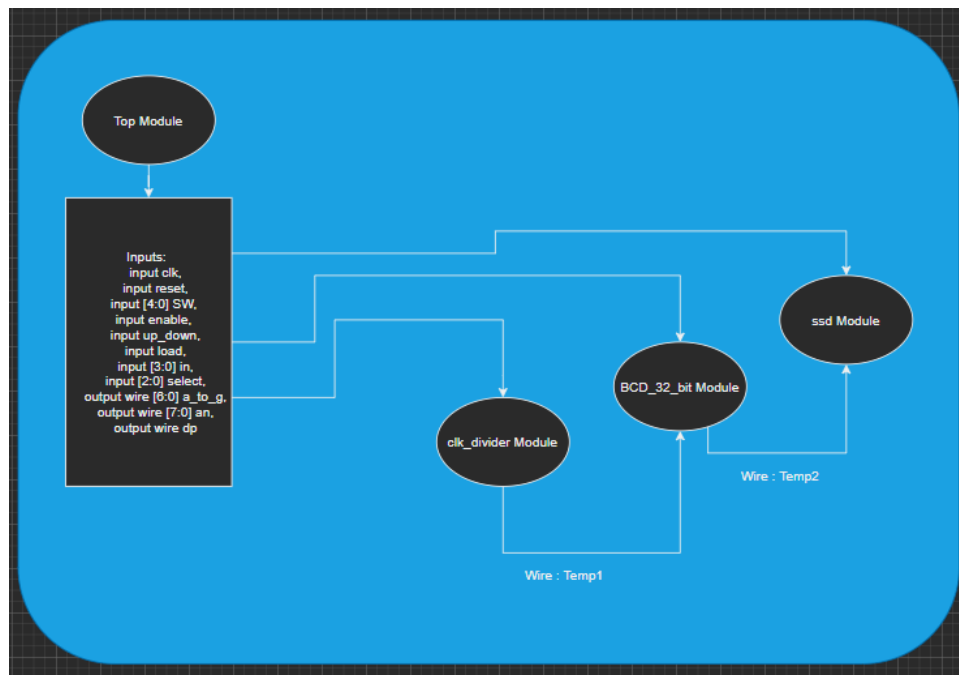


Figure 9: Top


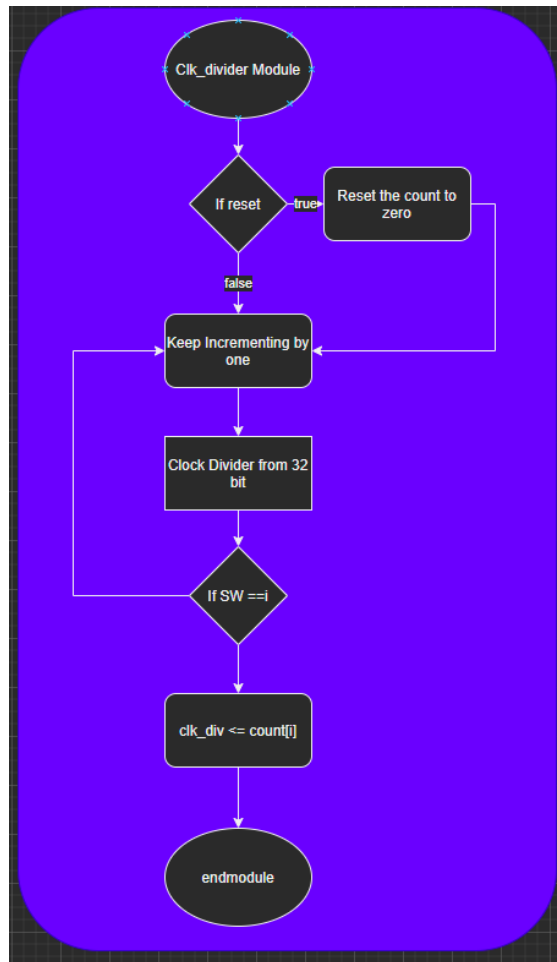


Figure 10: Clock divider

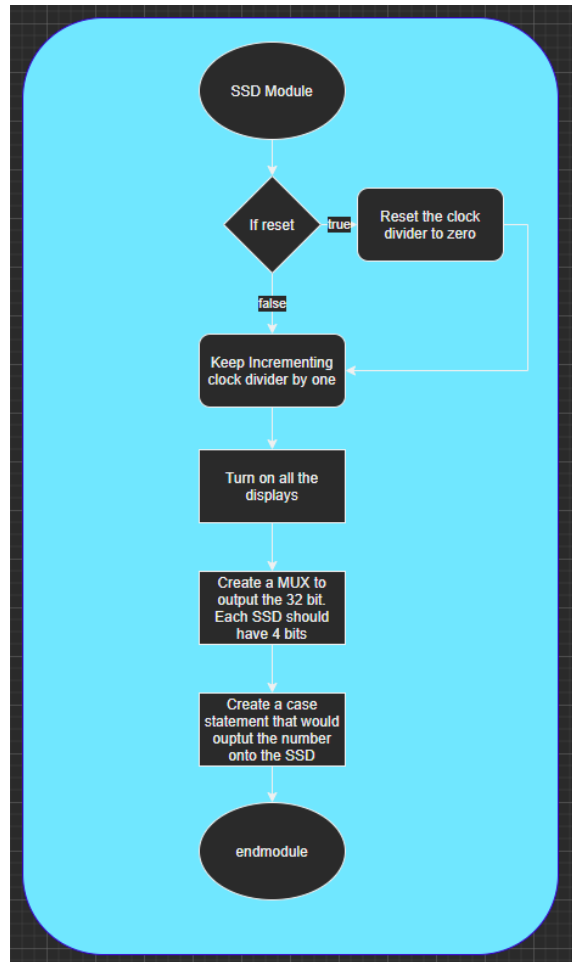

*Figure 11: Display*

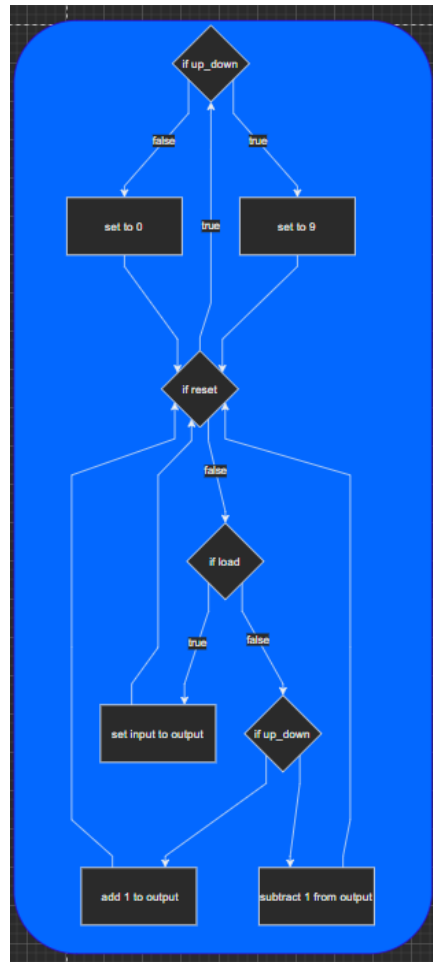


Figure 12: Counter

 


Figure 13: Demux

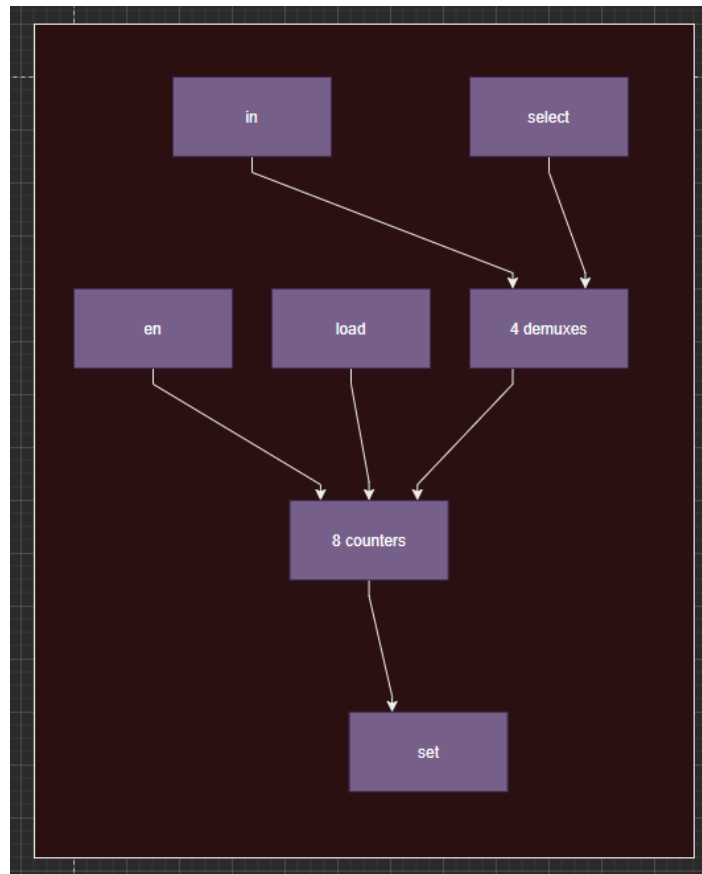


Figure 14: BCD 32 bit

## Results

 


Figure 15: Initial for Counting up

 


Figure 16: Result for Counting up

 


Figure 17: Initial for Counting down

 
 
 


Figure 18: Final Result for Counting Down

 




*Figure 19: Loading 3 at the 4th Seven Segment Display*



*Figure 20: Loading 7 at the 6th Seven Segment Display*



*Figure 21: Counting up from the load in*



 


Figure 22: Counting down from the load in

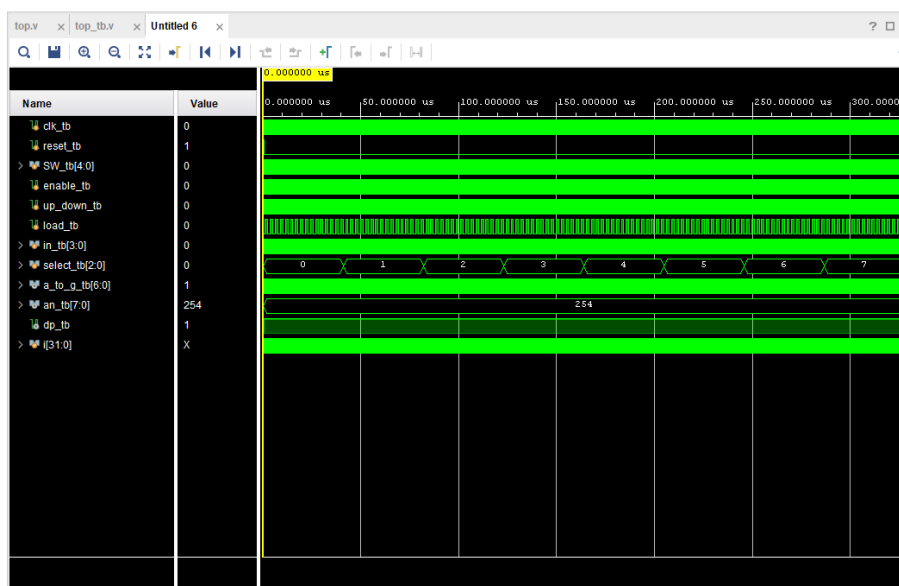


Figure 23: simulation zoomed to fit

 


Figure 23: Simulation zoomed in

Hierarchy							
Name	Slice LUTs (63400)	Slice Registers (126800)	F7 Muxes (31700)	Slice (15850)	LUT as Logic (63400)	Bonded IOB (210)	BUFGCTRL (32)
top	174	149	8	114	174	33	2
BCD (BCD_32_bit)	159	96	4	96	159	0	0
display (ssd)	5	20	0	9	5	0	0
GEN (clk_divider)	10	33	4	12	10	0	0

Figure 24: Utilization

## Discussion

The counter works without problems. There are no glitches in the display or inputs. Possible optimizations to the code could be made to improve performance, power dissipation, or complexity. Another possible feature could add a register that would hold the value of the loaded input, so we don't have to reset the other values of the counter to zero when we load in a value. That way, we could just load in a value mid count, and have it kept on doing what it is doing without resetting.

## Conclusion

We were able to accomplish all the objectives that were given in this lab. Given more time, adding a register to hold the value of the displays can be added relatively quickly.

## Work Distribution

Russell: everything / Philbert: everything / Paul: everything